

# Number System

## 1. Number System Conversion

- $$N = A_{n-1} \cdot r^{n-1} + A_{n-2} \cdot r^{n-2} + \dots + A_1 \cdot r + A_0 \cdot r^0 + \dots + A_{-m} \cdot r^{-m}$$

$n \rightarrow$  Most Significant Bit (MSB)

$m \rightarrow$  Least Significant Bit (LSB)

$r \rightarrow$  radix

- Binary ( $r = 2$ )


Octal ( $r = 8$ )

Decimal ( $r = 10$ )

Hexadecimal ( $r = 16$ )

- Decimal to Binary Conversion

**E.g.** Convert 119(10) to binary

 

**Solution:** 1110111(2)

**E.g.** Convert 0.75(10) to binary

Multiply 0.75 by 2     $(0.75)2=1.5$     1(MSB)

Multiply 0.75 by 2     $(0.5)2=1.0$     1

Multiply 0.75 by 2     $(0)2=0.0$     0(LSB)

**Solution** 0.110(2)

- Hexadecimal And Octal to Binary Conversion

E.g. 3 A (16)= 0011 1010 (2)

E.g. 2 7 (8) = 010 111 (2)

## 2. Binary Codes

- Signed Number Binary

Decimal	3	2	1	0	-1	-2	-3
Sign magnitude	0011	0010	0001	0000	1001	1010	1011
2s complement	0011	0010	0001	0000	1111	1110	1101
1s complement	0011	0010	0001	0000	1110	1101	1100

MSB为符号位;

原码->反码(1s):除符号位外全部取反;

反码->补码(2s):反码+1

- Gray code

Decimal	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
3-bit	000	001	011	010	110	111	101	100								
4-bit	0000	0001	0011	0010	0110	0111	0101	0100	1100	1101	1111	1110	1010	1011	1001	1000

二进制码→格雷码 (编码) :

此方法从对应的n位二进制码字中直接得到n位格雷码码字, 步骤如下:

- 对n位二进制的码字, 从右到左, 以0到n-1编号
- 如果二进制码字的第i位和i+1位相同, 则对应的格雷码的第i位为0, 否则为1 (当i+1=n时, 二进制码字的第n位被认为是0, 即第n-1位不变)

- Parity Method

- The parity method is a method of error detection for simple transmission errors involving one bit (or an odd number of bits).
- A parity bit is an "extra" bit attached to a group of bits to force the number of 1's to be either even (even parity偶校验) or odd (odd parity奇校验).

Example: The ASCII character for "a" is 1100001 and for "A" is 1000001. What is the correct bit to append to make both of these have odd parity?


The ASCII "a" has an odd number of bits that are equal to 1; therefore the parity bit is 0. The ASCII "A" has an even number of bits that are equal to 1; therefore the parity bit is 1.

# Boolean Switching Algebra



## 1. Logic Gates

- Tree Primitive Logic Gates: AND、OR、NOT



- AND

 

- OR

  


- NOT

  

- Derived Logic Gates: NAND、NOR、EX-OR、EX-NOR

- XOR:  $s = x \oplus y$

$$s = \bar{X}Y + X\bar{Y}$$

 

- NXOR:  $s = (x \oplus y)'$

$$s = XY + \bar{X}\bar{Y}$$

## 2. Switching Algebra Theorems

- Idempotency Property (幂等性):  $X + X = X$      $X \cdot X = X$
- Absorption Property(吸收):  $X + X \cdot Y = X$      $X \cdot (X + Y) = X$   
 $X + \overline{X} \cdot Y = X + Y$      $X \cdot (\overline{X} + Y) = X \cdot Y$
- De Morgan Properties(反演, 狄·摩根):  $\overline{X + Y} = \overline{X} \cdot \overline{Y}$      $\overline{X \cdot Y} = \overline{X} + \overline{Y}$
- Adjacency Properties:  $X \cdot Y + X \cdot \overline{Y} = X$      $(X + Y) \cdot (X + \overline{Y}) = X$

## 3. Karnaugh Maps

CD \ AB		AB			
		00	01	11	10
CD	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

- Simplification using K-map 2、3、4 variables

卡诺图化简逻辑函数的基本原理，是依据关系式  $A \cdot B + A \cdot \overline{B} = A$ ，即两个“与”项中，如果只有一个变量相反，其余变量均相同，则这两个“与”项可以合并成一项，消去其中互反的变量。

- 画卡诺圈所遵循的规则：
  - 必须包含所有的最小项；
  - 按照“从小到大”顺序，先圈孤立的“1”。再圈只能两个组合的，再圈四个组合的.....
  - 圈的圈数要尽可能少(乘积项总数要少)；
  - 圈要尽可能大(乘积项中含的因子最少)。

A \ BC		BC			
		00	01	11	10
A	0	1	1		
	1				

(a)  $F = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C = \overline{A} \overline{B}$


		BC			
		00	01	11	10
A	0				
	1	1	1	1	1

(b)  $F = A \bar{B} \bar{C} + A \bar{B} C + A B C + A B \bar{C} = A$

# Combinational Circuit Design
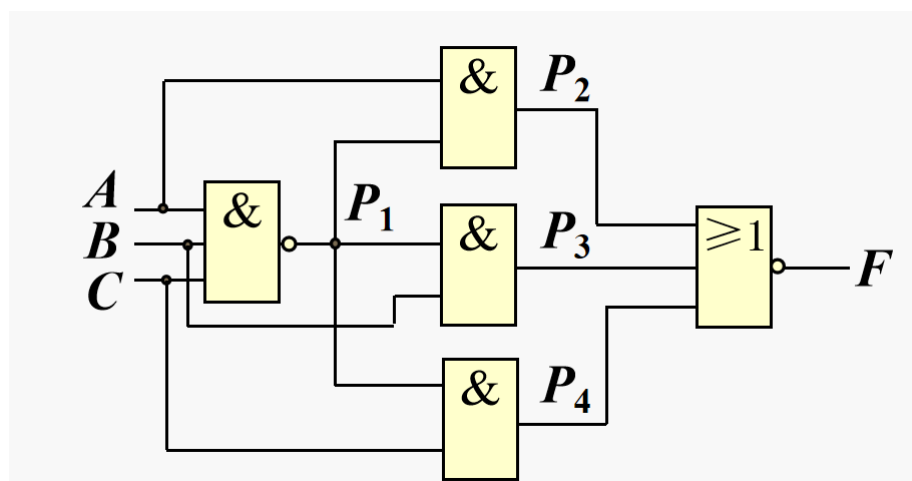
## 1. Analysis of Combinational Logic

- Deriving Switching Equations
- Simplifying the switching equations
- Giving truth table
- Logic function conclusion



Switching Equations:

$$P_1 = \overline{A \cdot B \cdot C}$$

$$P_2 = A \cdot P_1$$

$$P_3 = B \cdot P_1$$

$$P_4 = C \cdot P_1$$

$$F = \overline{P_2 + P_3 + P_4} = \overline{(A + B + C) \cdot \overline{A \cdot B \cdot C}}$$

Equations Simplified:

$$F = \bar{A} \cdot \bar{B} \cdot \bar{C} + A \cdot B \cdot C$$

Truth Table:

A	B	C	F
0	0	0	1
...	...	...	0
1	1	1	1

**Logic Function:**


agreement circuit

## 2. Combinational Circuit Design



 
## 3. Full Adder

- Combinational circuit that performs the additions of 3 bits (two bits and a carry-in bit)



 - A full adder can also be realized with two half adders and an OR gate



# 4. Binary Comparators

- Two-bit comparator


True Table:

A	B	$F_{A>B}$	$F_{A<B}$	$F_{A=B}$
0	0	0	0	1
0	1	0	1	0
1	0	1	0	0
1	1	0	0	1

$$F_{A>B} = A \cdot \overline{B} = A \cdot \overline{AB}$$

$$F_{A<B} = \overline{A} \cdot B = B \cdot \overline{AB}$$
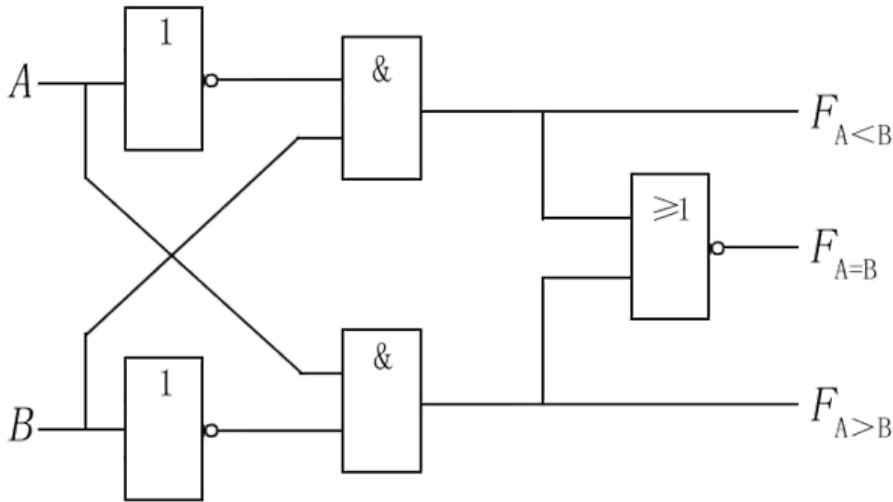
$$F_{A=B} = \overline{A} \cdot \overline{B} + A \cdot B = \overline{B \cdot \overline{AB} + A \cdot \overline{AB}}$$



- Multiple-bit comparators

$A_3 B_3$	$A_2 B_2$	$A_1 B_1$	$A_0 B_0$	$F_{A>B}$	$F_{A<B}$	$F_{A=B}$
$A_3 > B_3$	×	×	×	1	0	0
$A_3 < B_3$	×	×	×	0	1	0
$A_3 = B_3$	$A_2 > B_2$	×	×	1	0	0
$A_3 = B_3$	$A_2 < B_2$	×	×	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 > B_1$	×	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 < B_1$	×	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 > B_0$	1	0	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 < B_0$	0	1	0
$A_3 = B_3$	$A_2 = B_2$	$A_1 = B_1$	$A_0 = B_0$	0	0	1

## 5. Decoders

- 2 to 4 Decoders

Inputs			Outputs			
Enable G'	Select		Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>
	B	A				
H	X	X	H	H	H	H
L	L	L	L	H	H	H
L	L	H	H	L	H	H
L	H	L	H	H	L	H
L	H	H	H	H	H	L

- 3 to 8 Decoders

Inputs						Outputs							
Enable			Select										
G <sub>1</sub>	G <sub>2</sub> A'	G <sub>2</sub> B'	C	B	A	Y <sub>0</sub>	Y <sub>1</sub>	Y <sub>2</sub>	Y <sub>3</sub>	Y <sub>4</sub>	Y <sub>5</sub>	Y <sub>6</sub>	Y <sub>7</sub>
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	0	1	1	1	1	1	1	1
1	0	0	0	0	1	1	0	1	1	1	1	1	1
1	0	0	0	1	0	1	1	0	1	1	1	1	1
1	0	0	0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	0	0	1	1	1	1	0	1	1	1
1	0	0	1	0	1	1	1	1	1	1	0	1	1
1	0	0	1	1	0	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0

- Implementing Boolean functions using decoders

Use the decoder (74LS138) to implement the function

$$Y_1 = A'B' + AC + A'C'$$

$$Y_2 = A'C + AC'$$


$$Y_3 = B'C + BC'$$

$$Y_1 = A'B' + AC + A'C' = m_0 + m_1 + m_2 + m_5 + m_7 = \sum(0, 1, 2, 5, 7) = \prod(3, 4, 6) = m_3' m_4' m_6'$$

$$Y_2 = A'C + AC' = m_1 + m_3 + m_4 + m_6 = \sum(1, 3, 4, 6) = \prod(0, 2, 5, 7) = m_0' m_2' m_5' m_7'$$
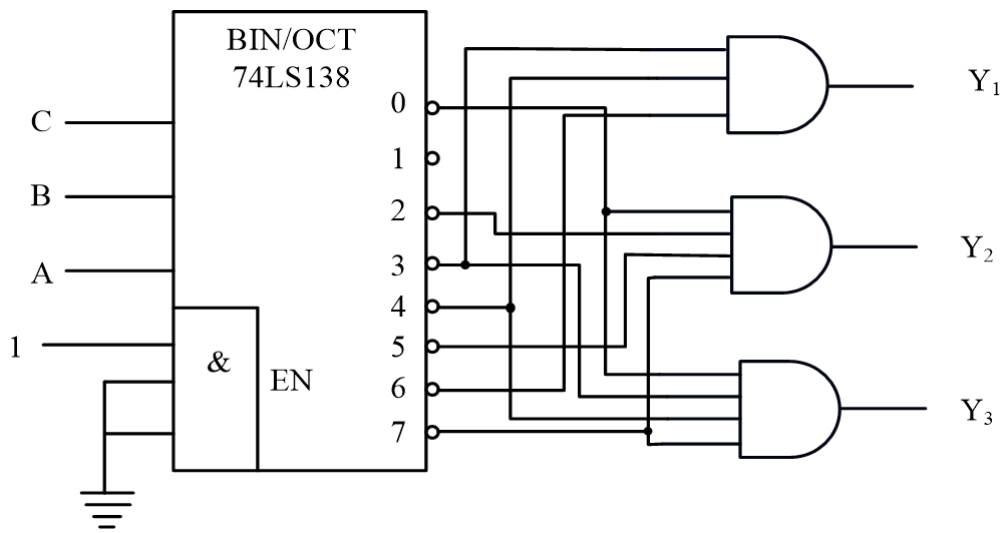
$$Y_3 = B'C + BC' = m_1 + m_2 + m_5 + m_6 = \sum(1, 2, 5, 6) = \prod(0, 3, 4, 7) = m_0' m_3' m_4' m_7'$$





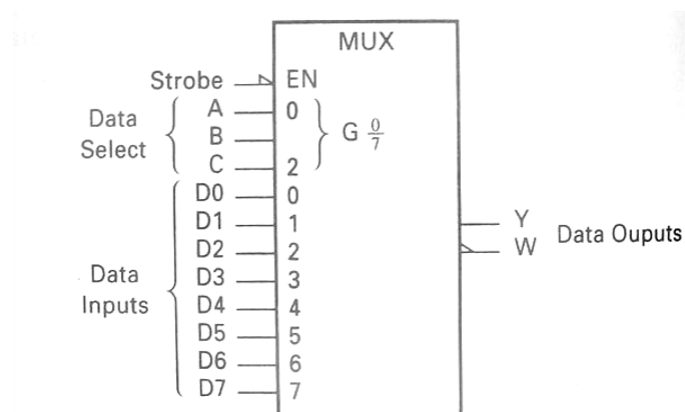
## 6. Endcoders

- MUX -> Multiplexers
- 8 to 1 MUX

$$Y = C'B'A'D_0 + C'B'AD_1 + C'BA'D_2 + C'BAD_3 + CB'A'D_4 + CB'AD_5 + CBA'D_6 + CBAD_7 = \sum_{i=0}^{2^n-1} m_i D_i$$




(b) IEEE logic symbol

- Implementing Boolean functions with Multiplexers

**Realize the Boolean function  $F=f(x,y,z)=\sum(1,2,4,5,7)$**

- Using 8 to 1 MUX

 


$$D_0 = D_3 = D_6 = 0$$

$$D_1 = D_2 = D_4 = D_5 = D_7 = 1$$

$$C = x, B = y, A = z$$

◦ Using 4 to 1 MUX

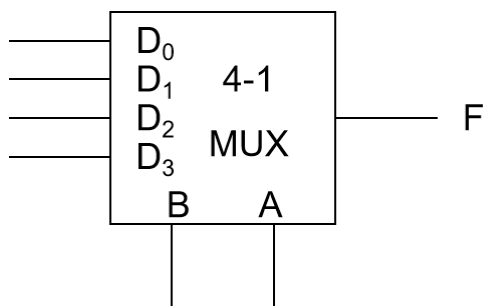

若  $A = Y, B = X$ , 则  $F = X'Y'D_0 + X'YD_1 + XY'D_2 + XYD_3$

XY		Z			
		00	01	11	10
Z	0		1		1
	1	1		1	1

其中, 根据卡诺图可得,  $D_0 = Z, D_1 = Z', D_2 = 1, D_3 = Z$

# Sequential Logic

## 1. Flip-Flops(FF)

- Type of FF:
  - SR
  - D
  - JK
- Type of Triggering
  - Untriggered (asynchronous 异步)
  - Level-triggered (C = 1)
  - Edge-triggered (rising or falling edge of C)
- SR latch
  - Characteristic Equation:  $Q^{n+1} = S + R' \cdot Q^n$  &&  $S \cdot R = 0$
  - True Table:

R	S	$Q^n$	$Q^{n+1}$	Function
0	0	0	0	Hold
0	0	1	1	Hold
0	1	0	1	Set
0	1	1	1	Set
1	0	0	0	Reset
1	0	1	0	Reset
1	1	0	0	Disallowed
1	1	1	0	Disallowed

- D latch
  - Characteristic Equation:  $Q^{n+1} = D$
  - True Table:

C	D	Next state of Q
0	X	No change
1	0	Q = 0; Reset state
1	1	Q = 1; Set state

- JK latch
  - Characteristic Equation:  $Q^{n+1} = JQ^n + K'Q^n$

- True Table:


J	K	$Q^n$	$Q^{n+1}$	Function
0	0	0	0	Hold
0	0	1	1	Hold
0	1	0	0	Reset
0	1	1	0	Reset
1	0	0	1	Set
1	0	1	1	Set
1	1	0	1	Toggle
1	1	1	0	Toggle
 
## 2. State Diagram

- Mealy model




When at state s1 and apply input I, we get output O and proceed to state s2.



- Moore model




 When at state s1 with output O1 and apply input I, we proceed to state s2 with Output O2.



### 3. Synchronous Sequential Circuit Analysis

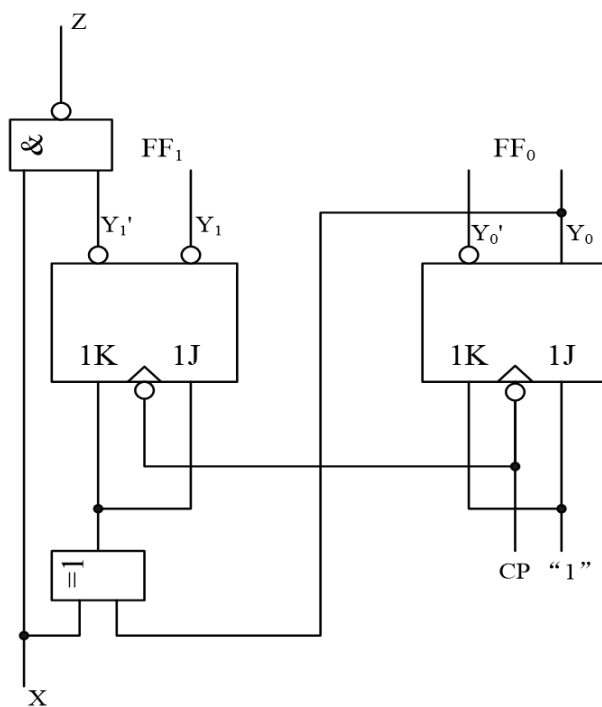- 1.Determine the system variables: input, state, and output
- 2.Determine the flip-flop type. Write the characteristic equations
- 3.write the excitation equations
- 4.write the next state equations
- 5.Write the output variable equations
- 6.Construct a transition table
- 7.Assign symbols to the states and construct a table or state diagram
- 8.When possible, construct a timing diagram
- 9.Functionality analysis)



Analysis the following synchronous sequential circuit, suppose the present state is 00, the input sequence is 0000011111, give the timing diagram.

- input = X
- output = Z
- state variables =  $Y_1$  and  $Y_2$
- $Y^{n+1} = JY^n + K'Y^n$

- $K_0 = J_0 = 1$   
 $K_1 = J_1 = X \oplus Y_0$
- $Y_0^{n+1} = Y_0'$   
 $Y_1^{n+1} = X'Y_1'Y_0 + X'Y_1Y_0' + XY_1'Y_0' + XY_1Y_0$
- $Z = (XY_1')' = X' + Y_1$

		X	
		0	1
Y <sub>1</sub> Y <sub>0</sub>	00	0	1
	01	1	0
	02	0	1
	03	1	0

$Y_1^{n+1}$  K-Map

		X	
		0	1
Y <sub>1</sub> Y <sub>0</sub>	00	1	1
	01	0	0
	02	0	0
	03	1	1

$Y_0^{n+1}$  K-Map


		X	
		0	1
Y <sub>1</sub> Y <sub>0</sub>	00	1	0
	01	1	0
	02	1	1
	03	1	1


Z K-Map

Transition table:

Present state Y <sub>1</sub> Y <sub>0</sub>	Next state x/z	
	X=0	X=1
	Y <sub>1</sub> <sup>+</sup> Y <sub>0</sub> <sup>+</sup> / Z	Y <sub>1</sub> <sup>+</sup> Y <sub>0</sub> <sup>+</sup> / Z
00	01/1	11/0
01	10/1	00/0
11	00/1	10/1
10	11/1	01/1


 
- ■ Q1 - 00
- Q2 - 01
- Q3 - 11
- Q4 - 10



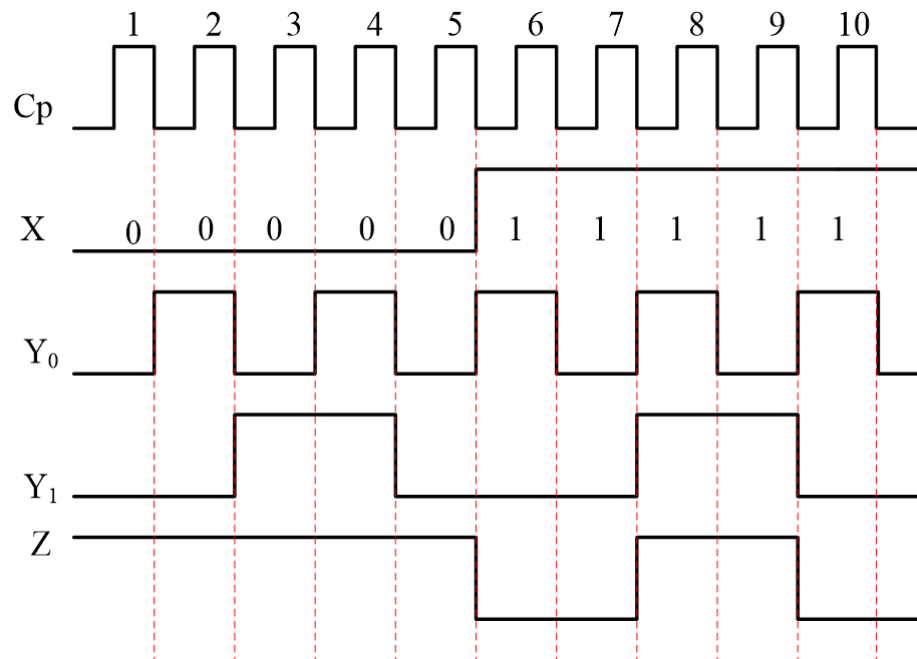

## 4. Asynchronous Counters

- Three bit Asynchronous Counter

  

- Asynchronous Decade Counter(异步十进制计数器)


This counter uses partial decoding to recycle the count sequence to zero after the 1001 state.









$Q_3 Q_2 Q_1$	$Q_3 + Q_2 + Q_1 +$	$D_3 D_2 D_1$	$Z$
000	111	111	0
001	000	000	1
010	ddd	ddd	d
011	ddd	ddd	d
100	ddd	ddd	d
101	ddd	ddd	d
110	001	001	0
111	110	110	0

 

$$D_3 = Q_3' Q_1' + Q_3 Q_1$$

$$D_2 = Q_3' Q_1' + Q_3 Q_1$$

$$D_1 = Q_1'$$

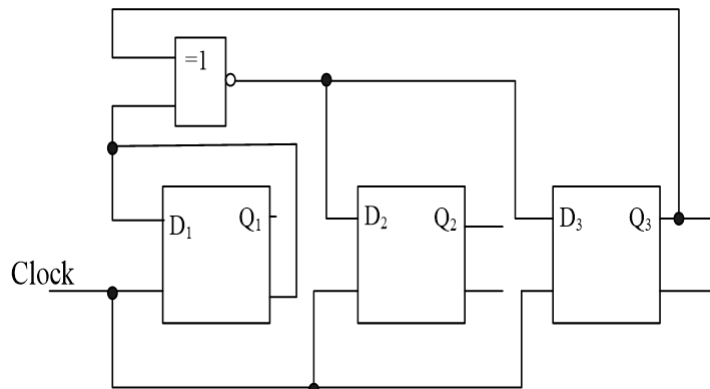 


**Example2:Construct a Mealy state diagram that will detect a serial input sequence of 10110. The detection of the required bit pattern can occur in a longer data string and the correct pattern can overlap with another pattern. When the input pattern has been detected, cause an output z to be asserted high.**

*For example, let the input string be*


$x = 10110110110$

$z = 00001001001$

 


## 6. Registers

- Serial-in/Serial-out Shift Register

 

- Shift Registers Counters

- Johnson Register

 

- Ring Register

